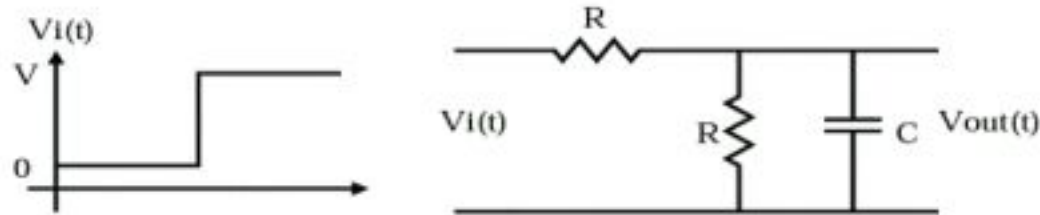


Analog Guide


Raja Reddy P, Indian Institute of Science

July 26, 2007

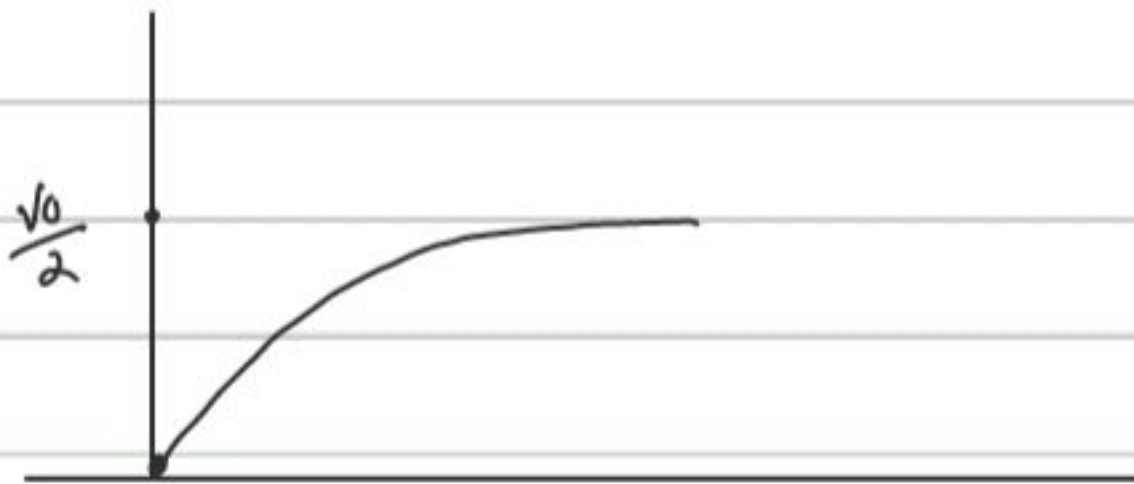1. Calculate $V_{out}(s)/V_{in}(s)$. plot $V_o(t)$. calculate time constant and pole frequency.





$$\begin{aligned} \frac{V_{out}(s)}{V_{in}(s)} &= \frac{\frac{R}{1+RCs}}{R + \frac{R}{1+RCs}} = \frac{R}{2R + RCs} \\ &= \frac{1}{2 + RCs} = \frac{1}{RC \left(1 + \frac{2}{RC} \right)} \end{aligned}$$



$$\begin{aligned} V_o(s) &= \frac{V_o}{s(2 + RCs)} = \frac{V_o/2}{s \left(1 + \frac{RC}{2} \right)} \\ &= \frac{V_o}{2} (1 - e^{-t/\tau}) \quad \tau = \frac{RC}{2} \end{aligned}$$

pole = $-2/RC$

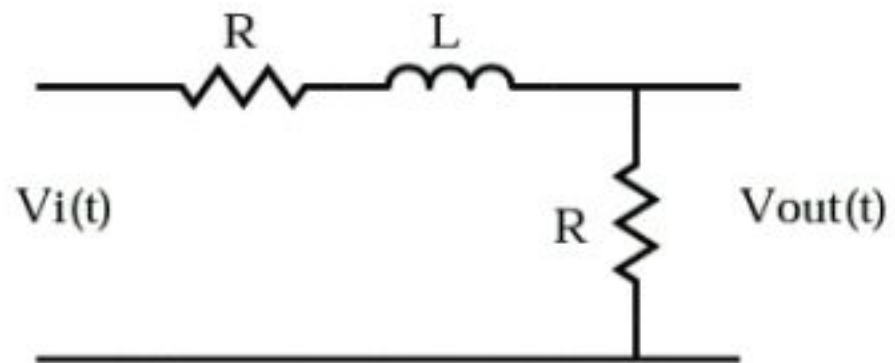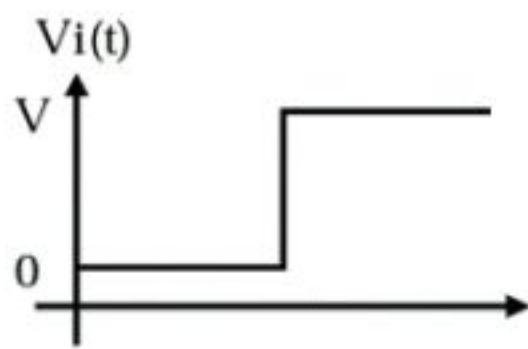2. In the following circuit plot $i_L(t)$, $V_L(t)$




$$V_{out}(t) = \frac{V_0}{2} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{2R}$$

$$i_L(t) = \frac{V_0}{2R} (1 - e^{-t/\tau})$$


$$V_L(t) = L \frac{di_L(t)}{dt} = L \frac{V_0}{2R} \frac{1}{\tau} e^{-t/\tau}$$

$$= \frac{L V_0}{2R} \frac{2R}{L} e^{-t/\tau} = \underline{\underline{V_0 e^{-t/\tau}}}$$

3. Find $V_o(t)$ in the circuit below.

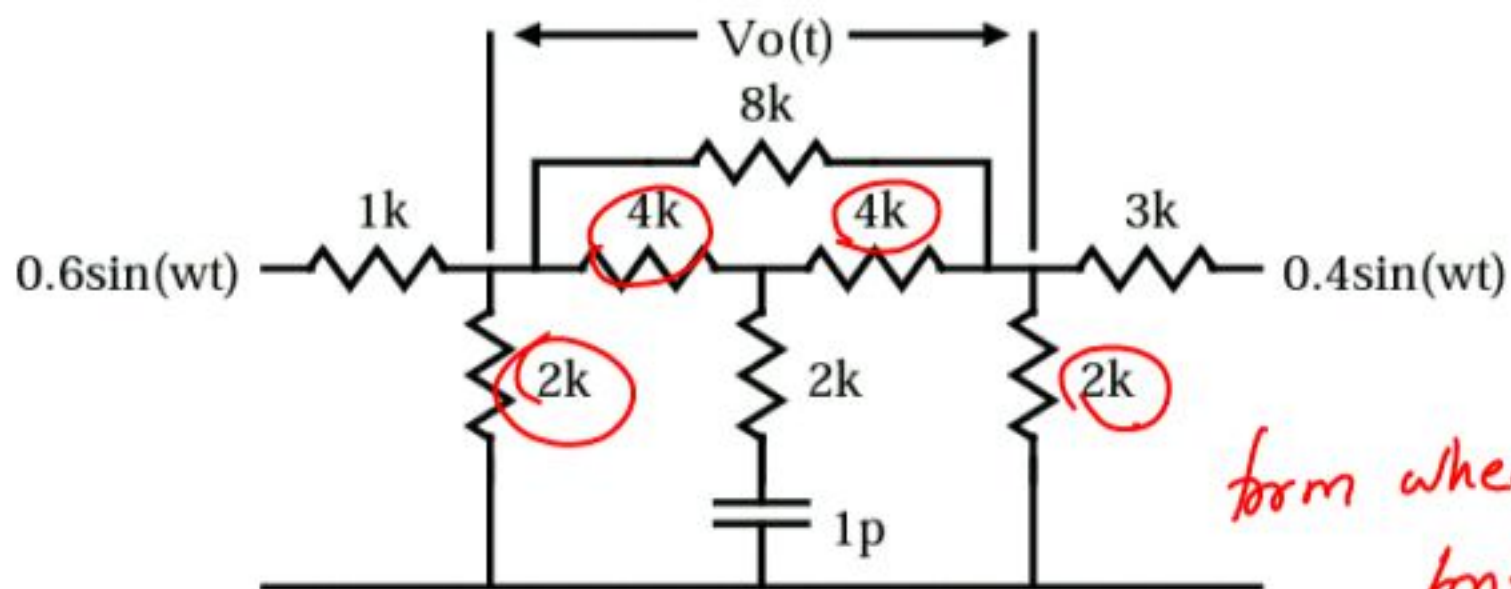

form wheatstone bridge

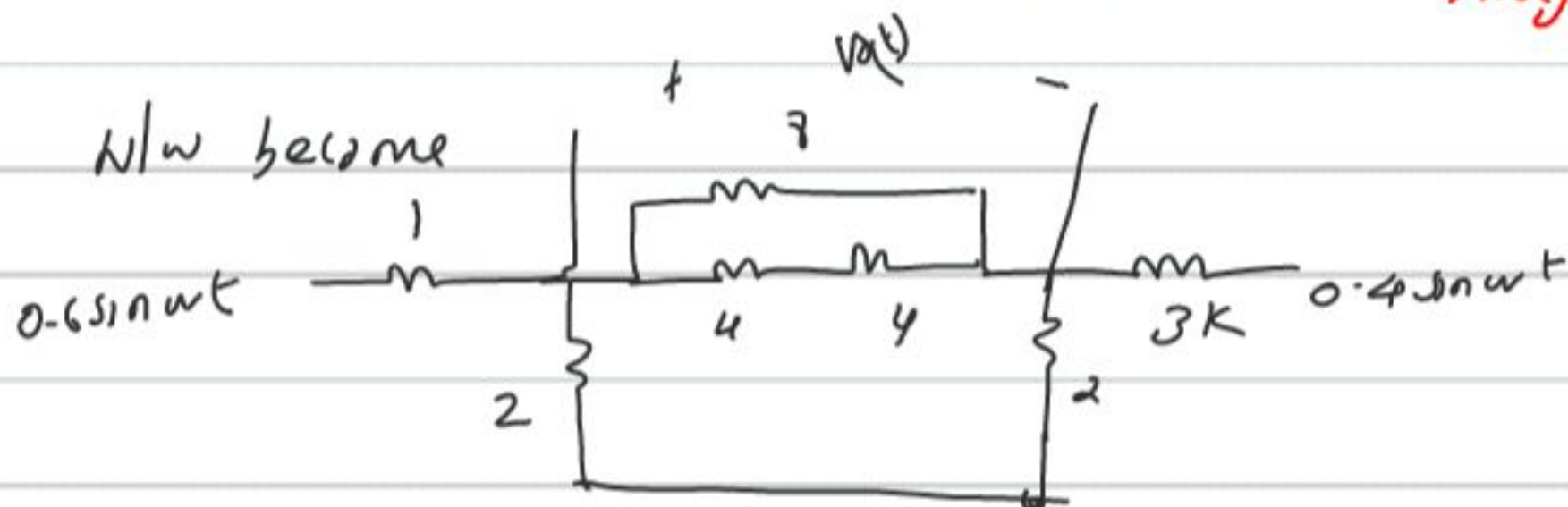

≈ 1.5

4. A system has an SNR of 60 dB. If an uncorrelated noise of 1 mV is added in a 1V of signal to it, then what is the SNR?

$$SNR_{in} = 10 \log \left(\frac{1^2}{(10^{-3})^2} \right)$$


$$= 10 \log (10^6) = \underline{\underline{60 \text{ dB}}}$$

$$\frac{SNR_{out}}{SNR_{in}} = 10^6$$

$$SNR_{out} = 10^6 \times 10^6 = 10^{12}$$

$$\Rightarrow \underline{\underline{120 \text{ dB}}}$$

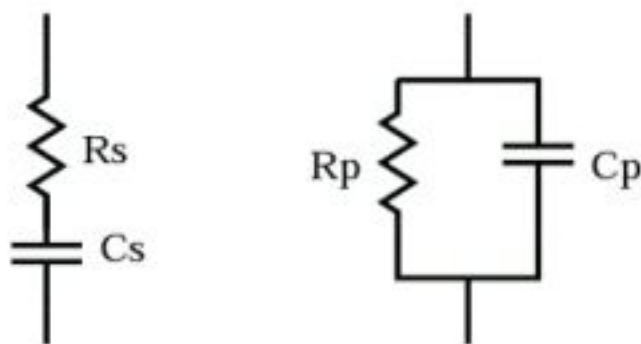
5. Both ckts are equivalent. Express R_p and C_p in terms of R_s and C_s . Find ω range for which these both are equivalent. Assume high quality factor.



$$R_p = R_s (1 + Q^2)$$

$$C_p = \frac{C_s Q^2}{1 + Q^2}$$

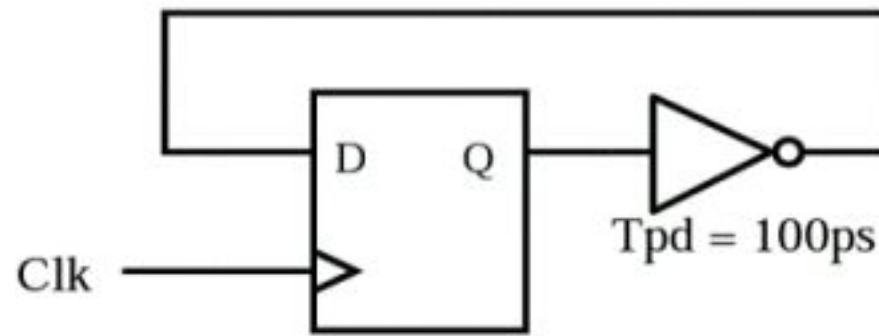6. Calculate the maximum clock frequency.



$$T_{cq} = 1\text{ns}$$



$$T_{\text{setup}} = 200\text{ps}$$

$$T_{\text{hold}} = 300\text{ps}$$



$$T \geq t_{cq} + t_{\text{logic}} + t_{\text{setup}}$$

$$\geq 1 + 0.1 + 0.2 = \underline{\underline{1.3\text{ ns}}}$$

7. Plot V_{out} .

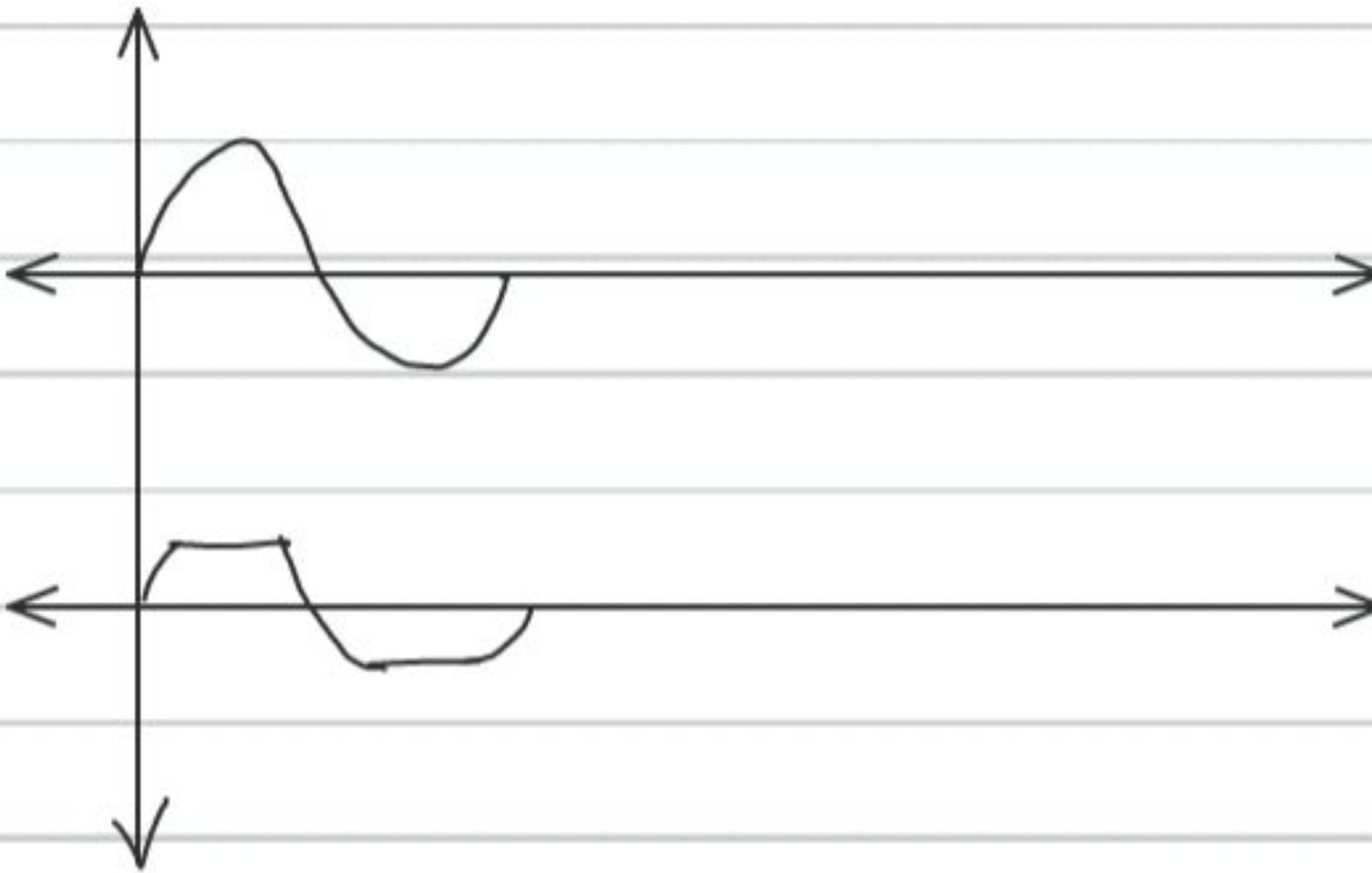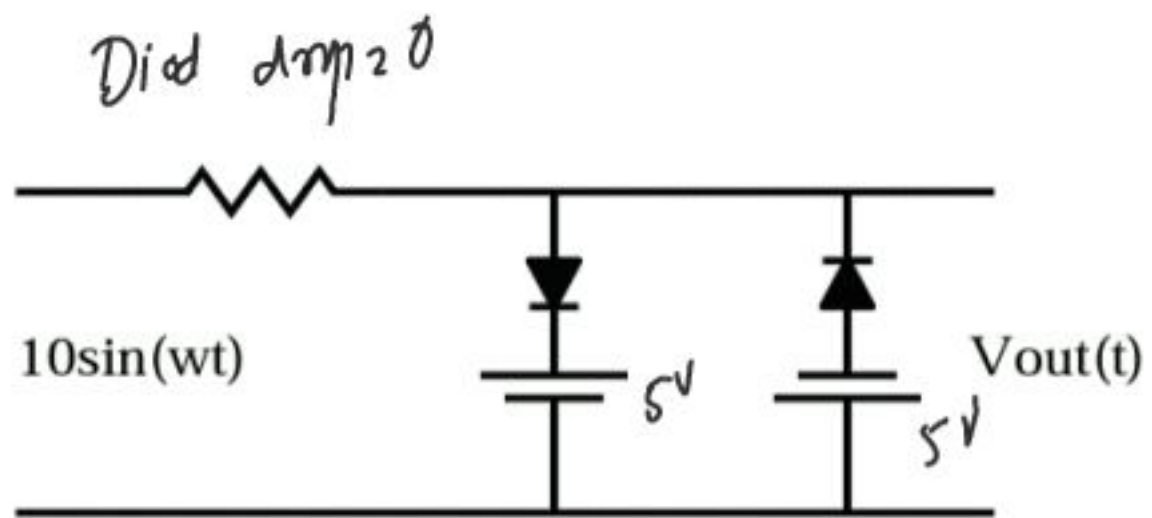


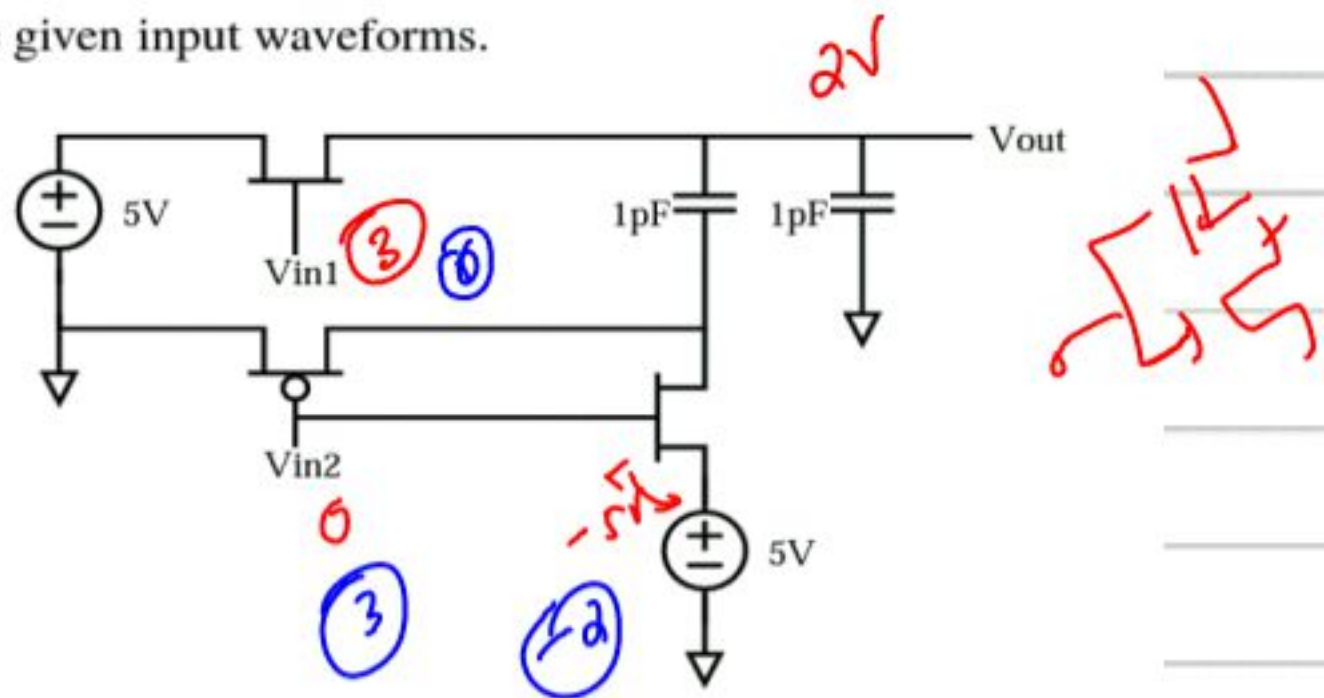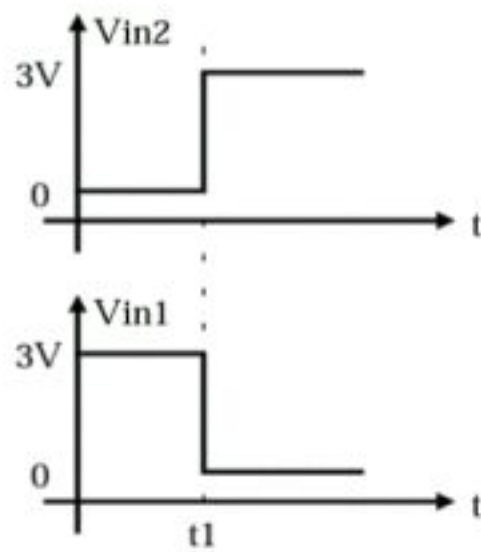8. Plot V_{out} with respect to the given input waveforms.






9. Design a divide-by-3 counter using D-flipflops. The duty cycle of the divided clock should be $2/3$.

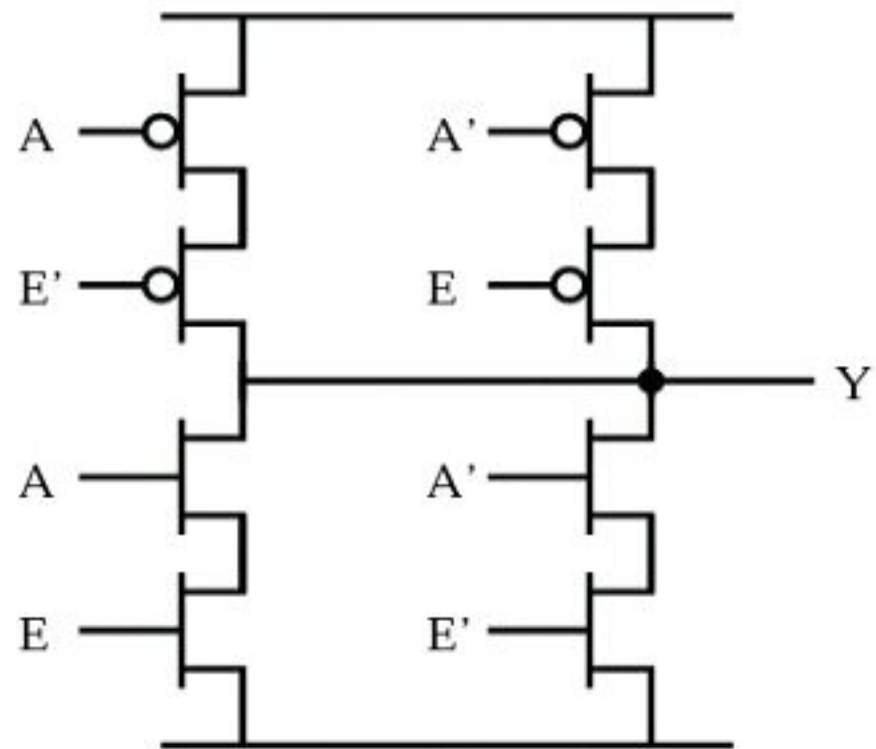10. What is the function of the following circuit?



XOR gate

11. Plot the output V_{out} .

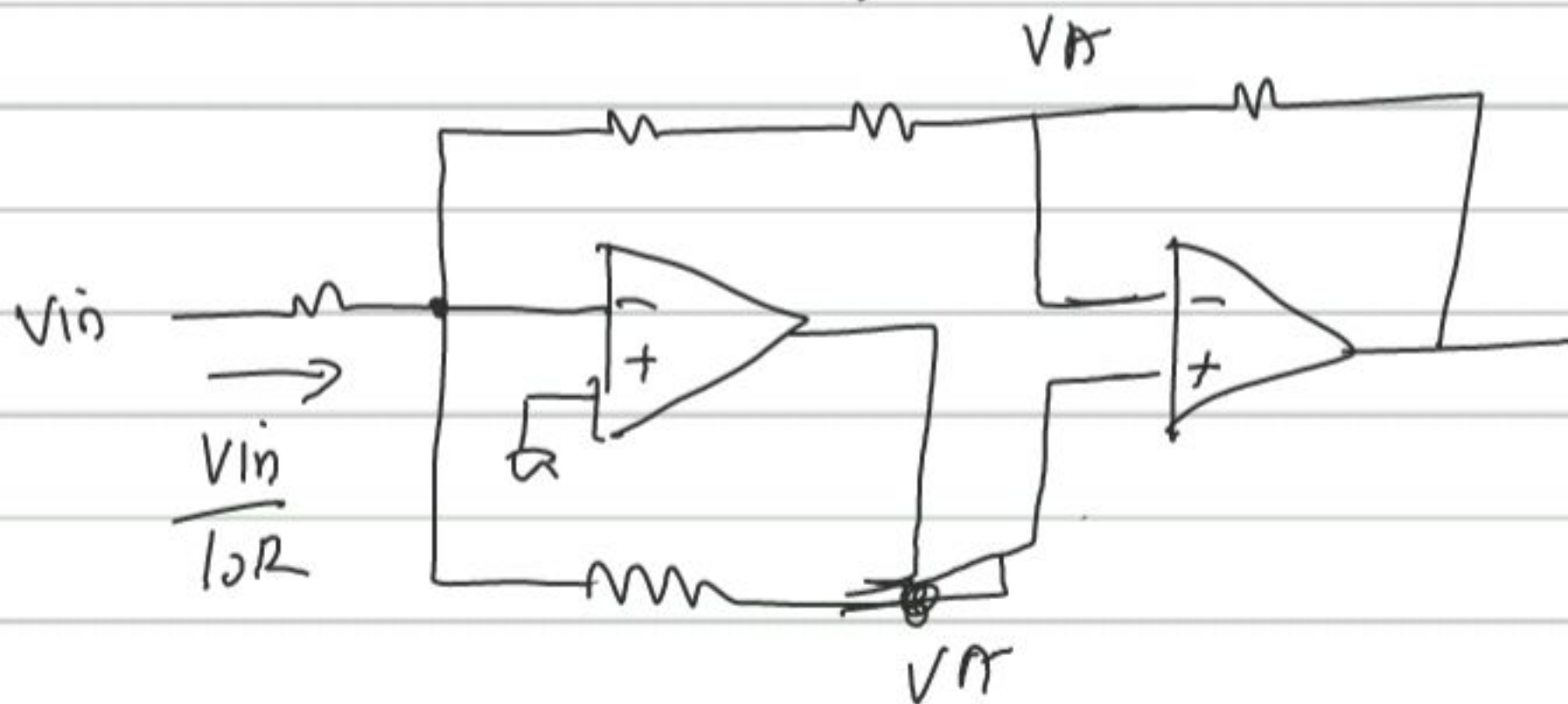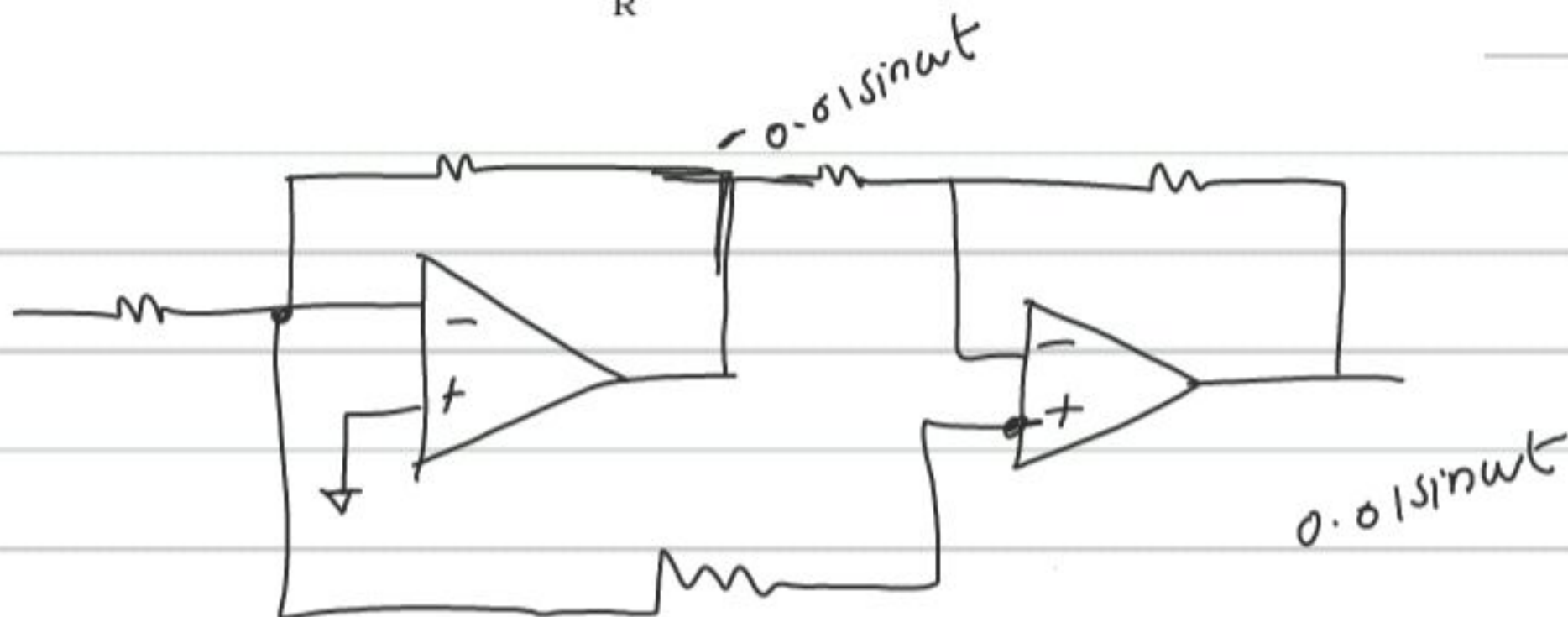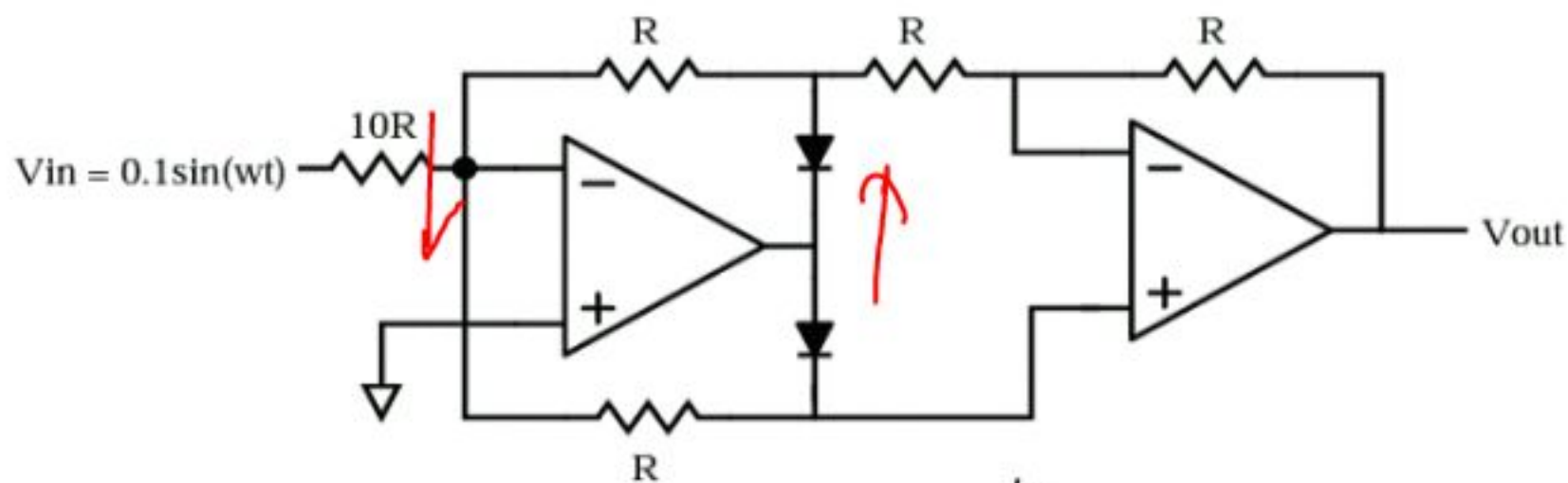

$$-\frac{V_A}{2R} + \frac{V_A}{R} = \frac{V_{in}}{10R}$$


$$1.5 V_A = -\frac{V_{in}}{10}$$

$$V_A = -\frac{V_{in}}{15}$$

$$\frac{-V_{in}}{2R/5} = \frac{V_{out} - V_{in}}{R}$$

$$\frac{V_{in}}{30R} + \frac{V_{in}}{R} = \frac{V_{out}}{R}$$

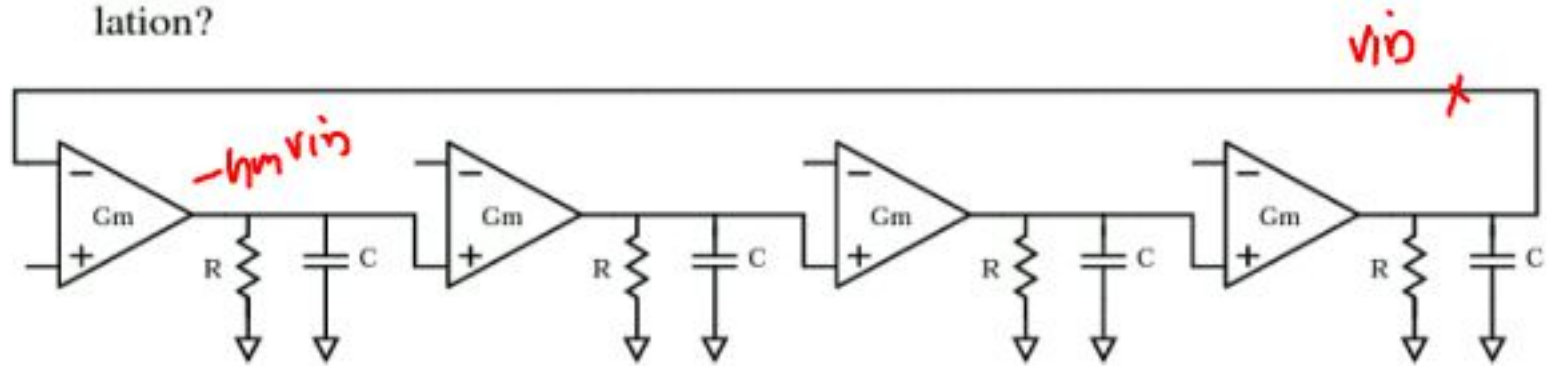12. Calculate the frequency of oscillation. What is the minimum required G_m for oscillation?



$$-\left(\frac{gmR}{1+RCs}\right)^4 = 1$$

$$-(gmR)^4 = (1+RCs)^4$$

$$= (1 + R^2C^2s^2 + 2RCs)^2$$

$$= 1 + R^4C^4s^4 + 4R^2C^2s^2 +$$

$$2R^2C^2s^2 + 4R^3Cs^3 + 4RCs$$

$$1 + (gmR)^4 + R^4C^4\omega^4 - 6R^2C^2\omega^2 + j\omega^3R^3C^3 + j4\omega RC = 0$$

$$j4\omega RC = 0$$

$$\omega^3 R^3 C^3 = \omega RC$$

$$\omega^2 = \frac{1}{R^2C^2}$$


$$\omega = \frac{1}{RC}$$

$$\left| \frac{umR}{1+j} \right|^4 = 1$$


$$\left| \frac{umR}{\sqrt{2}} \right|^4 = 1$$

$$\underline{\underline{umR = \sqrt{2}}}$$

13. Calculate the output impedance.

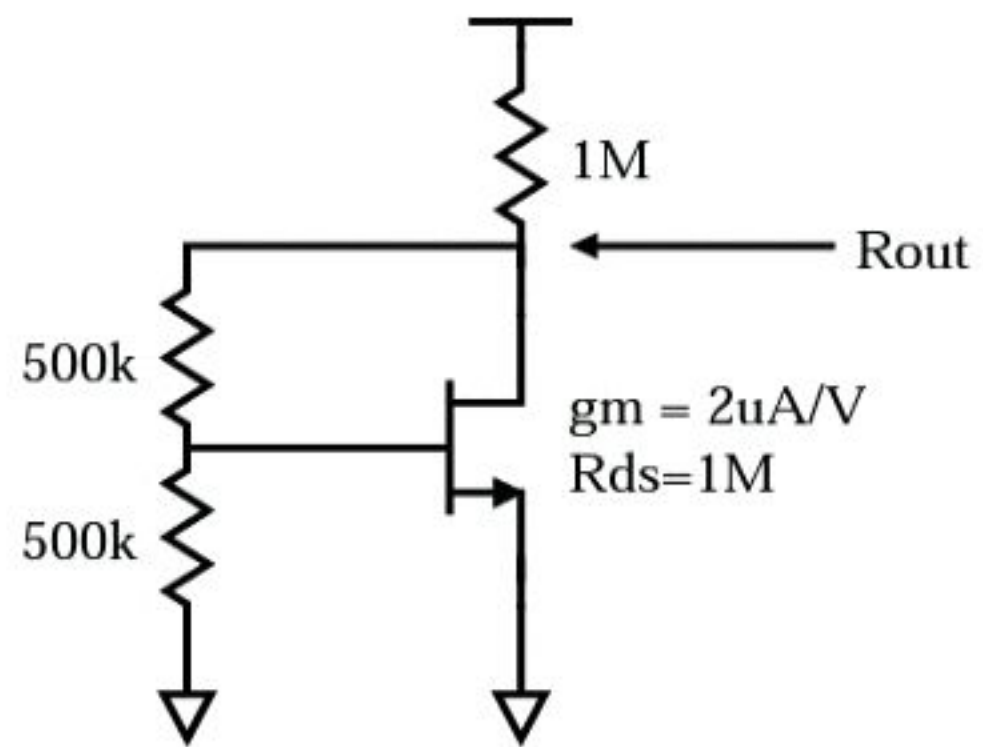


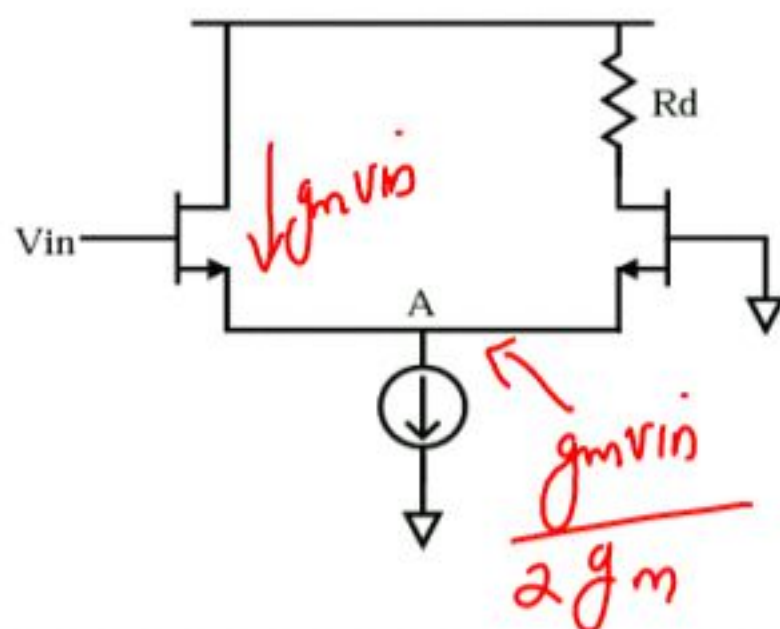14. Both transistors are biased in saturation. Calculate " V_A/V_{in} ". Neglect the body effect.



$$\frac{V_A}{V_{in}} = \frac{1}{2}$$

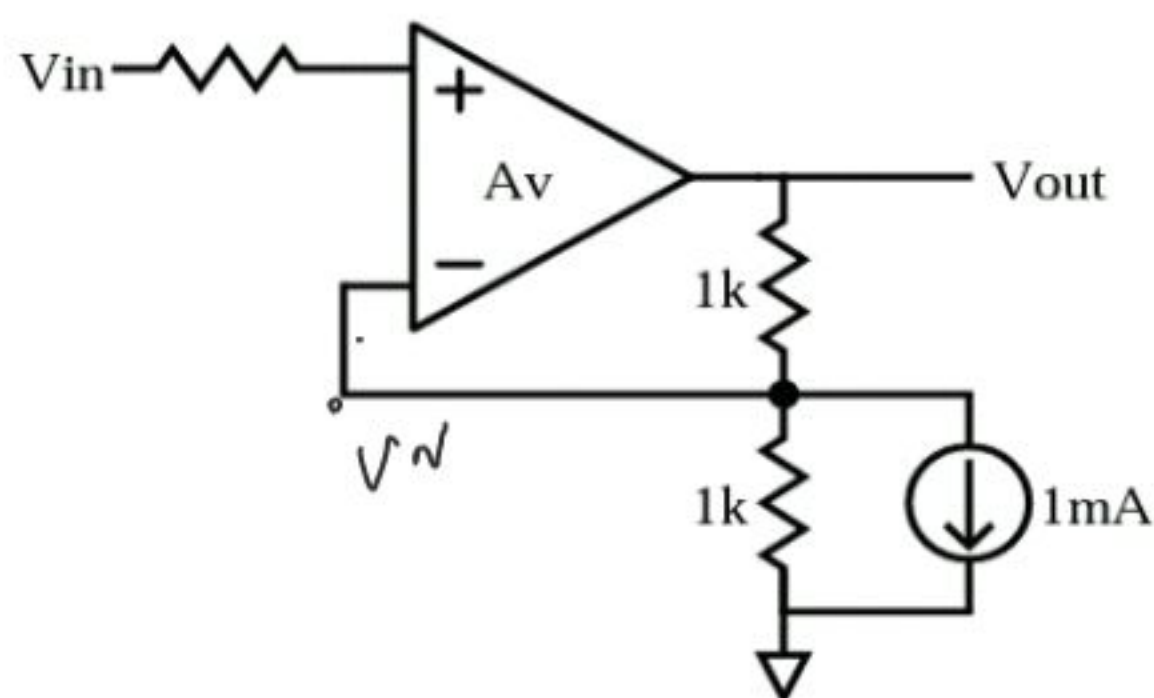15. Calculate the output if (i) gain $A_v = \text{infinity}$ (ii) gain $A_v = 10$



$$(i) \quad \frac{V_{in}}{1k} + 1mA + \frac{V_N - V_{out}}{1k} = 0$$

$$2V_N + 1 = V_{out}$$

$$(ii) \quad V_N + 1 + V_N - V_{out} = 0$$

$$V_{out} = 2V_N + 1$$

$$A(V_N - V_{out}) = V_{out}$$

$$V_N - V_{out} = \frac{V_{out}}{10}$$

$$V_N = V_{out} - \frac{V_{out}}{10}$$

$$V_{out} = 2\left(V_{out} - \frac{V_{out}}{10}\right) + 1$$


$$= 2V_{out} + 1 - \frac{V_{out}}{5}$$

$$\left(1 + \frac{1}{5}\right) v_{out} = 2v_{in} + 1$$



$$\frac{6}{5} v_{out} = 2v_{in} + 1$$

$$v_{out} = \frac{10}{6} v_{in} + \frac{5}{6}$$

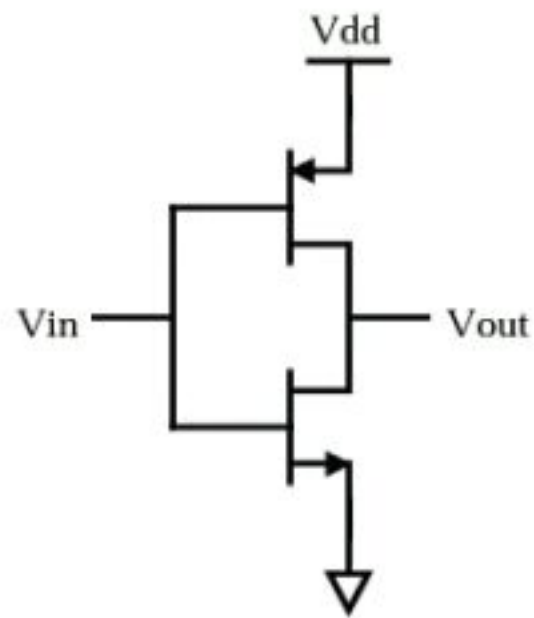
16. If the following inverter biased in the middle of V_{dd} , what is the small signal gain?
(Answer: $g_m r_o$)



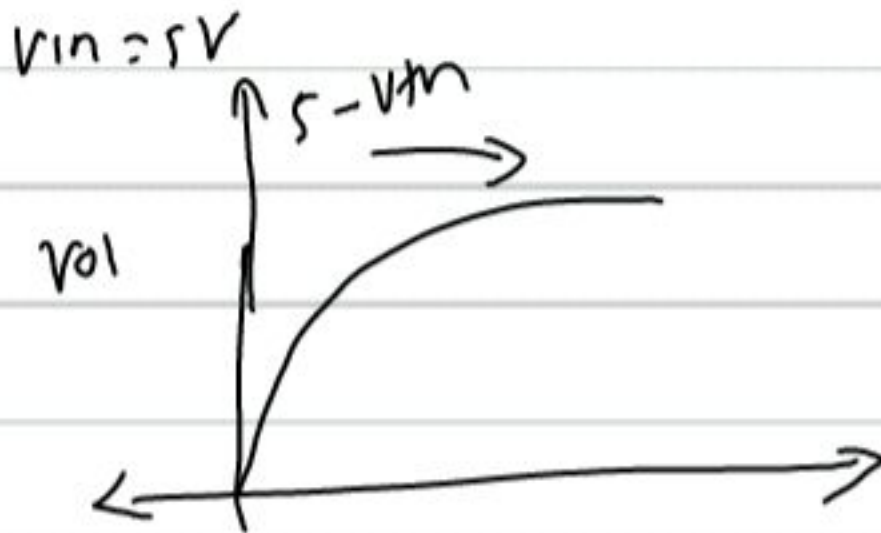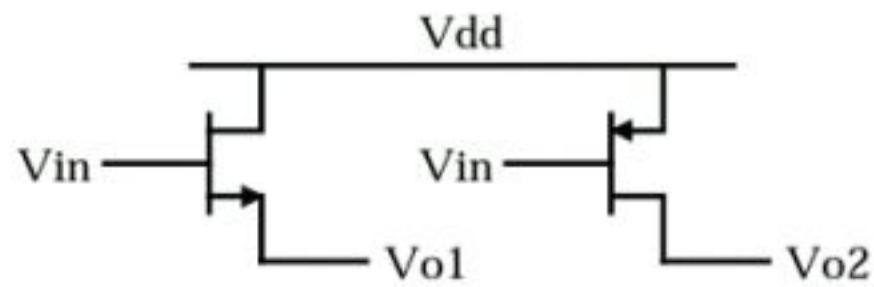
22. For the following circuits, $V_{dd}=5V$, tell me what are V_{o1} and V_{o2} when V_{in} is 5V, 3V, 2.5V and 0V.



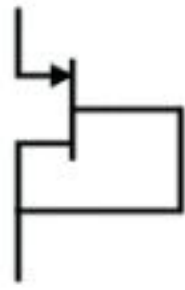23. What are the effective resistance from source to drain of the following two transistors? (The value of the resistance is R). Answer: both of them are $1/g_m$.




(a)

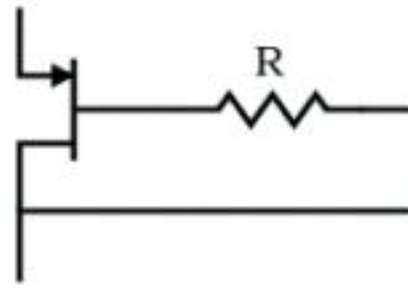

(b)

Both $1/g_m$



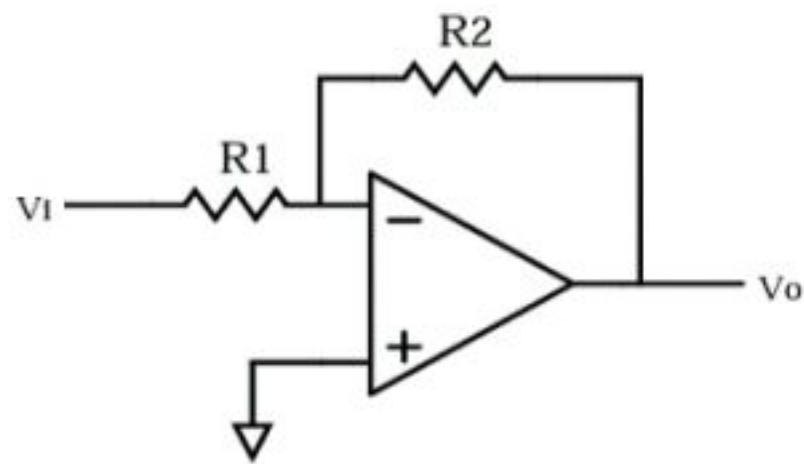
24. In the following figure, if the two resistors are equal, what is its -3dB bandwidth? Compare its stability with that of a source follower.



$$\omega_{3dB} = \omega_u \times \frac{R_1}{R_1 + R_2}$$

$\omega_u =$ unity gain
B.W

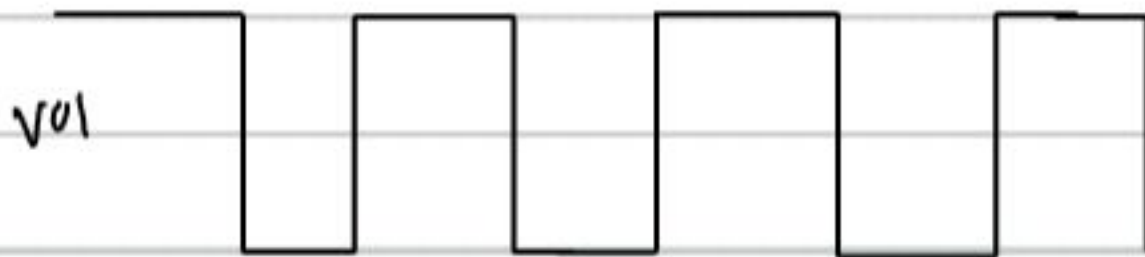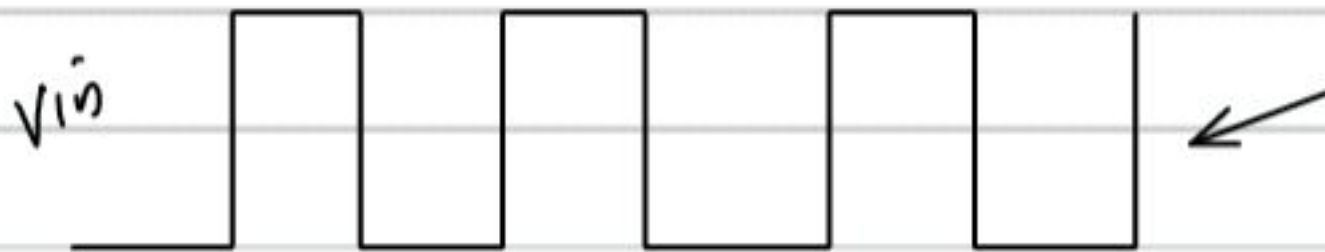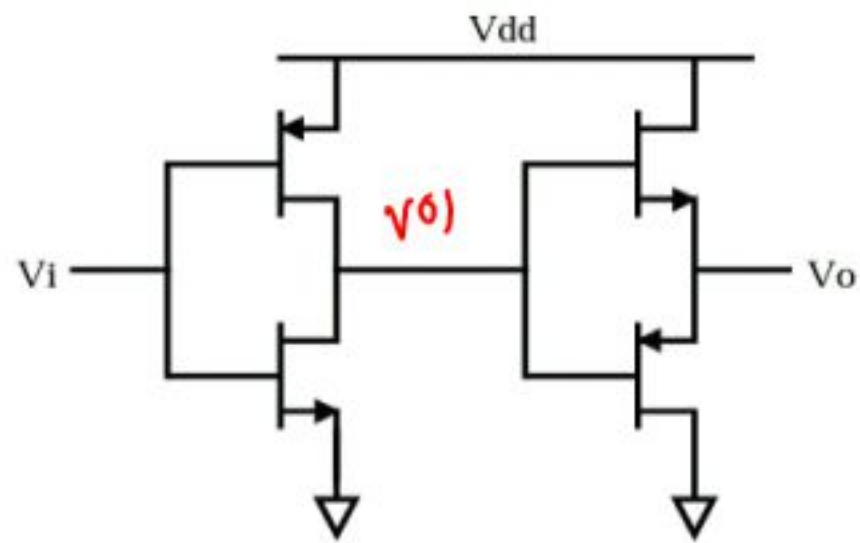25. For the following circuit, if the input is a rail-to-rail square wave, plot the wave after the inverter and v_o .



$V_{DD} - V_{thN} \rightarrow$

v_{mp}

