

32

33

34

35

36

37 ☆

38

39

40

41

42

QUESTION: 37 GROUP: Hardware SECTION: Analog Circuits
Mark(s): 1

For an opAmp the common mode gain = 6, if common mode rejection ratio is 25dB, what is differential mode voltage gain?

☐ 150

☒ 106.7

☐ 19

☐ 6.16

Previous Question

Next Question

ASUS VivoBook

QUESTION: 5 GROUP: Aptitude SECTION: Puzzles

Mark(s): 1

If $(P@Q)$ means P is son of Q, $(P\&Q)$ means P is mother of Q, $(P\$Q)$ means P is brother of Q and $(P=Q)$ means P is father of Q. In $(M\&N)\$O$ and $(O\$S)=T$ how is M related to T?

☐ Sister-in-law

☐ Niece

☐ Sister

☐ Aunt

[Previous Question](#)

[Next Question](#)

ASUS VivoBook

1

2

3 ☆

5

6

7

8

9

10

11

12

- (I) Ajit's last name is not Pandey but he is a Network engineer and he does not play either Violin or Piano.
- (II) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (III) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (IV) Java developer is working in Chennai and his name is not Pankaj.
- (V) Singh does not play Flute.
- (VI) The person who is working in Chennai plays Piano.

Question:

Who is the Java developer?

☐ Pandey

☐ Sha

☒ Singh

☐ Naik

Previous Question

Next Question

ASUS VivoBook

QUESTION: 5 GROUP: Aptitude SECTION: Puzzles

Mark(s): 1

If $(P@Q)$ means P is son of Q, $(P\&Q)$ means P is mother of Q, $(P\$Q)$ means P is brother of Q and $(P=Q)$ means P is father of Q. In $(M\&N)\$O$ and $(O\$S=T)$ how is M related to T?

☐ Sister-in-law

☐ Niece

☐ Sister

☒ Aunt

[Previous Question](#)

[Next Question](#)

ASUS VivoBook

1

2

3 ☆

5

6

7

8

9

10

11

12

- (I) Ajit's last name is not Pandey but he is a Network engineer and he does not play either Violin or Piano.
- (II) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (III) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (IV) Java developer is working in Chennai and his name is not Pankaj.
- (V) Singh does not play Flute.
- (VI) The person who is working in Chennai plays Piano.

Question:

Who is the Java developer?

☐ Pandey☐ Sha☒ Singh☐ Naik[Previous Question](#)[Next Question](#)

ASUS VivoBook

1 ☆

2

3

4

5

6

7

8

9

10

11

12

- (I) Ajit's last name is not Pandey but he is a Network engineer and he does not play Flute.
- (II) .Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (III) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (IV) Java developer is working in Chennai and his name is not Pankaj.
- (V) Singh does not play Flute.
- (VI) The person who is working in Chennai plays Piano.

Question:

Who plays Flute?

☐ Amit

☒ Ajit

☐ Sunil

☐ Pankaj

Previous Question

Next Question

ASUS VivoBook



QUESTION 1 GROUP: Aptitude SECTION: Logical Reasoning

Marks: 1

Direction: Read the following information and answer the question that follows.

Four software professionals (one is Amit) working in IT industry in different cities (Jaipur is also one of the city) on different domains have a hobby of playing different musical instruments.

Below are the some details:

- (i) Ajit's last name is not Pandey but he is a Network engineer and he does not play either Guitar or Piano.
- (ii) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (iii) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (iv) Java developer is working in Chennai and his name is not Pankaj.
- (v) Singh does not play Flute.
- (vi) The person who is working in Chennai plays Piano.

Question:

Who plays Flute?

Previous Question

Next Question

ASUS VivoBook

1 ☆

2

3

4

5

6

7

8

9

10

11

12

- (I) Ajit's last name is not Pandey but he is a Network engineer and he does not play Flute.
- (II) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (III) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (IV) Java developer is working in Chennai and his name is not Pankaj.
- (V) Singh does not play Flute.
- (VI) The person who is working in Chennai plays Piano.

Question:

Who plays Flute?

☐ Amit

☐ Sunil

☐ Pankaj

Previous Question

Next Question

ASUS VivoBook

41

42

43

44

45 ☆

46

47

ORG : H, 2007

CLR : C

MOV : B, #number1

ADD : B, #number2

MOV : DPTB, 2008H

MOVX J: @DPTB, B

HLT : "Exit program"

E8H

A2H

QUESTION: 47 GROUP: Hardware SECTION: Basic Electronics

Mark(s): 1

The total KVAR of a 6-step bank of 3 phase capacitors is 400 KVAR. Each step has equal power rating. The operating voltage of the bank is 440 V. The making capacity of the contactor used is 1148 A and the peak current for switching the capacitor bank is 3.1 kA. What is the operating current of the contactor used and inductance required to limit the peak current? Assume the safety factor to be 1.43.

☐ 125.09 A, 0.083 H

☐ 200 A, 0.1 H

☐ 500 A, 1 H

☐ 239 A, 2.1 H

47 ☆

48

49

Previous Question

Next Question

ASUS Vivobook



QUESTION 1 GROUP: Aptitude SECTION: Logical Reasoning
Mark(s): 1

Direction: Read the following information and answer the question that follows.

Four software professionals (one is Amit) working in IT industry in different cities (Jaipur is also one of the city) on different domains have a hobby of playing different musical instruments.

Below are the some details:

- (i) Ajit's last name is not Pandey but he is a network engineer and he does not play either Guitar or Piano.
- (ii) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (iii) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (iv) Java developer is working in Chennai and his name is not Pankaj.
- (v) Singh does not play Flute.
- (vi) The person who is working in Chennai plays Piano.

Question:
Who plays Flute?

Previous Question Next Question

ASUS VivoBook

QUESTION: 44 GROUP: Hardware SECTION: Signals and Systems

Marks: 1

The system $y(n) = x(n) \cdot u(n)$ has the properties of:

☐ Nonlinearity, Causality, and Time Variant

☐ Linearity, Noncausality, and Time Variant

☐ Linearity, Causality, and Time Invariant

☒ Linearity, Causality, and Time Variant

Previous Question

Next Question

ASUS VivoBook

Marks: 1

For 8085 microprocessor programming, Determine the output of the following addition program- Number 1= 81H & Number 2= 37H

```
ORG 1000H
MVI A, 81H
MVI B, 37H
ADD B, A
MVI C, 00H
MVI D, 00H
MVI E, 00H
HLT
```

- ☐ E8H
- ☐ A2H
- ☐ B8H
- ☐ C9H

Previous Question Next Question

ASUS VivoBook

QUESTION: 46 GROUP: Hardware SECTION: Digital Electronics

Mark(s): 1

An overhead water tank has two sensors, A situated at bottom of tank and B at the top. The sensors indicate 1 when water is below the sensors and 0 when it is above. A D latch based with input grounded is used to turn on and off the motor to fill water to the tank. The latch has two asynchronous inputs set and reset. What logic circuit must be connected to set and reset input so as to generate suitable control signals for the motor?

☐ Set = $A+B$ reset = $(A+B)'$

☐ Set = $A+B$ reset = AB

☐ Set = AB reset = $A'B'$

☐ Set = AB reset = $A+B'$

Previous Question

Next Question

ASUS VivoBook

QUESTION: 42 GROUP: Hardware SECTION: Analog Circuits

Marks: 1

Compared to conventional CMOS comparators, the BiCMOS comparators is preferred as it provides

☐ High bandwidth

☒ High speed

☐ High gain

☐ High precision

Previous Question

Next Question

ASUS VivoBook

QUESTION: 40 GROUP: Hardware SECTION: Basic Electronics

Mark(s): 1

What will be the percentage change of intrinsic carrier concentration of germanium for per degree rise in temperature?

☐ 4.6%

☐ 3.5%

☒ 5.5%

☐ 4.53%

Previous Question

Next Question

ASUS VivoBook

Mark(s) 1

34

35

36

37

38

39 ☆

40

41

42

43

44

Which one of the following correctly implements the object of uvm object based class?

☐ function void set_config_object (string inst_name,
string field_name,
uvm_object value)

☐ function void set_config_object (int inst_name,
string field_name,
uvm_object value)

☐ function void get_config_object (string inst_name,
string field_name,
uvm_object value, bit clone = 1)

☐ function void set_config_object (string inst_name,
string field_name,
uvm_object value, bit clone = 1)

[Previous Question](#)[Next Question](#)

ASUS VivoBook

38

39

40

41

42

43 ☆

44

45

46

47

48

QUESTION: 43 GROUP: Hardware SECTION: Digital Electronics

Mark(s): 1

A counter has two T flip flops TA and TB. Outputs QA and QB. TA=QB and TB=QA. What is the counting sequence?

☒ 0210,0213

☐ 0321,0321

☐ 3210,3210

☐ 0320,320

Previous Question

Next Question

ASUS VivoBook

33

34

35

36

37

38 ☆

39

40

41

42

43

```
function void set_inst_override_by_type
(
    ovm_object_wrapper original_type,
    string full_inst_path
)
```

```
function void set_inst_override_by_type
(
    ovm_object_wrapper original_type,
    ovm_object_wrapper override_type,
    string full_inst_path
)
```

```
function void override
(
    ovm_object_override_type
)
```

Previous Question

Next Question

ASUS VivoBook

31

QUESTION 36 GROUP: Hardware SECTION: Analog Circuits

Mark(s): 1

32

33

34

35

36 ☆

37


38

39

40

41

42

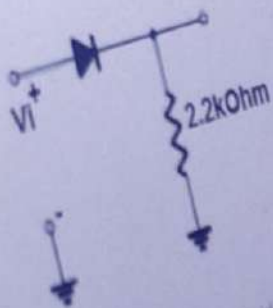

A silicon diode of threshold voltage $0.7V$ is connected as shown. What is the maximum amplitude of input voltage if the dc voltage obtained is $2.2V$?

☐ 3.65V☐ 2.9V☐ 7.3V[Previous Question](#)[Next Question](#)

ASUS VivoBook

36

37

38

39

40

41 ☆

42

43

44

45

46

QUESTION: 41 GROUP: Hardware SECTION: RTL

Mark(s): 1

The mobility of electron & hole of CMOS inverter is given by $545 \text{ cm}^2/\text{Vs}$ & $130 \text{ cm}^2/\text{Vs}$ respectively. $V_{DD}=2.5 \text{ volt}$ & $V_{thn}=0.6 \text{ volt}$. Find the average of rise & fall time for the cases when the ratio of width of PMOS to NMOS is $W_p/W_n=1$.

☐ 82.3 pico second

☐ 92.3 pico second

☐ 72.3 pico second

☐ 62.3 pico second

Previous Question

Next Question

ASUS VivoBook

QUESTION: 48 GROUP: Hardware SECTION: Microprocessors and Microcomputers

Mark(s): 1

The microprocessor system communicates with peripherals via

☒ The address bus

☐ A keyboard

☐ Input and output ports

☐ Read only memories

Previous Question

Next Question

ASUS VivoBook

21


QUESTION: 24 GROUP: Hardware SECTION: Digital Electronics

22

Marks: 1
The minimum Boolean for the following circuit is:

23

24 ☆

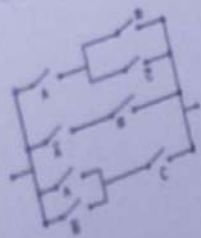

25

26

27

28

29

30

31

☐ $A + B + C$

☐ $A + B$

☐ $AB + AC + BC$

☐ $A + BC$

[Previous Question](#)[Next Question](#)

ASUS VivoBook

QUESTION: 17 GROUP: Aptitude SECTION: Puzzles

Mark(s): 1

Which of the following will replace the question mark (?) in the following sequence so that it will complete the sequence?

M81L K270 ? G3U

☐ H9S

☐ J9S

☐ J18R

☒ I9R

Previous Question

Next Question

ASUS VivoBook

QUESTION: 20 GROUP: Aptitude SECTION: Problem Solving

Marks: 1

N is a number when divided by 11, 17 and 19 leaves remainders 7, 13 and 15 respectively. What will be the remainder when the least such number is divided by 23?

☐ 5

☐ 13

☐ 11

☒ 7

Previous Question

Next Question

ASUS VivoBook

QUESTION: 18 GROUP: Aptitude SECTION: Puzzles

Marks: 1

In a code language, NATIONAL is coded as 13292915. How would you code ORGANIZE in the same language?

☐ 31330823

☒ 31082333

☐ 08322333

☐ 31083323

[Previous Question](#)

[Next Question](#)

ASUS VivoBook

QUESTION: 50 GROUP: Hardware SECTION: Semiconductor Physics

Mark(s): 1

In case of Semiconductor memories, which logic family work on negative logic?

☒ ECL

☐ CMOS

☐ TTL

☐ PMOS

Previous Question

Next Question

ASUS VivoBook

QUESTION: 15 GROUP: Aptitude SECTION: Problem Solving

Mark(s): 1

A mixture of 150 litres contains milk and water in the ratio 8 : 7. How much more water should be added to get a new mixture containing milk and water in the ratio 4 : 5?

☐ 15 litres

☒ 30 litres

☐ 10 litres

☐ 20 litres

Previous Question

Next Question

ASUS VivoBook

QUESTION: 16 GROUP: Aptitude SECTION: Problem Solving

Mark(s): 1

The total age of all the guests in the party was 540 years. If a South Indian couple (guests) left the party, then the average age of the remaining guests still remained unchanged, where the age of both the husband and wife (the South Indian couple) was same, then the average age of this couple and the total number of guests in the party, respectively, can be

☒ 20 years, 27

☐ Cannot be determined

☐ 15 years, 38

☐ 18 years, 27

[Previous Question](#)

[Next Question](#)

ASUS VivoBook

QUESTION 13 GROUP: Aptitude SECTION: Data Sufficiency

8

Mark(s): 1

9

10

11

12

13 ☆

14

15

16

17

18

Direction: Question is followed by two statements I and II. Answer the question using the following instructions:

Mark A) if the question can be answered by one of the statements alone but not by the other

Mark B) if the question can be answered by using either statement alone

Mark C) if the question can be answered using both statements together, but cannot be answered using either statements alone

Mark D) if the question cannot be answered even by using both statements together

Is Anup older than Reema?

- (I) Nazneen's age is half the age of Mehak, who is four years older than Reema.
- (II) Anup is older than Nazneen by 12 years.

(C)

(D)

(A)

(B)

Previous Question

Next Question

ASUS VivoBook

QUESTION: 19 GROUP: Aptitude SECTION: Problem Solving

Marks: 1

Fifty cows can graze a field for 40 days and 40 cows can graze the same field for 80 days. Some grass is already there and it grows at a constant rate. For how many days can 60 cows graze the same field? (The growth of grass is also there.)

☐ 20.66 days

☐ 25.66 days

☐ 30.65 days

☒ 26.66 days

Previous Question

Next Question

ASUS VivoBook

9

Mark(s) 1

10

11

12

13

14 ☆

15

16

17

18

19

20

Direction: The question is followed by two statements (I) and (II). Answer the question using the following instructions.

Mark (A) if the question can be answered by one of the statements alone but not by the other.

Mark (B) if the question can be answered by using either statement alone.

Mark (C) if the question can be answered using both statements together, but can not be answered using either statements alone.

Mark (D) if the question cannot be answered.

Is Suman elder than James?

I) Suman is four years older than Khushi, who is two years younger than Manas

II) James is three years older than Manas

☐ (D)☐ (B)☐ (A)[Previous Question](#)[Next Question](#)

ASUS VivoBook

7

8

9

10

11

12 ☆

13

14

15

16

17

QUESTION: 12 GROUP: Aptitude SECTION: Problem Solving

Mark(s): 1

Consider a number 5789. Form all the possible permutations of this number by changing the order of its digits in it. Add these permutations to get a number A. How many of nine multiples of 1111 less than 10000 divide A?

☐ 4

☒ 3

☐ 3

☐ 6

[Previous Question](#)
[Next Question](#)

ASUS VivoBook

6

7

8

9

10

11 ☆

12

13

14

15

16

QUESTION: 11 GROUP: Aptitude SECTION: Problem Solving

Mark(s): 1

A gardener had a number of shrubs to plant in rows. At first, he tried to plant 8, then 12 and then 16 in a row but he always had three shrubs left with him. On trying seven shrubs, he was left with none. Find the total number of shrubs.

☐ 51

☒ 147

☐ 99

☐ 163

[Previous Question](#)
[Next Question](#)

ASUS VivoBook

		16	15	16
	Super Cab	19	18	20
	Travel Home	15	18	18
	One Call	14	15	12
	Drive Home	18	16	17
	King Cab	18	18	17
	Others	100	100	100
	Total			

Question:

If the market growth is 20% every month, then find the ratio of revenue of 'Drive Home' from Jan 2012 to Feb 2012, if the total revenue of the market in the month of January is Rs. 27.5 million?

☐ 7:15

☒ 7:9

☐ 2:3

☐ 14:15

[Previous Question](#)

[Next Question](#)

ASUS VivoBook

Service providers	Jan'2012	Feb'2012	Mar'2012
Super Cab	16	15	16
Travel Home	19	18	20
One Call	15	18	18
Drive Home	14	15	12
King Cab	18	16	17
Others	18	18	17
Total	100	100	100

Question:

What percentage of revenue of Travel Home in Mar'2012 is more than the revenue of 'Drive Home' in the same month?

☐ 50%

☐ 48.48%

☐ 33.33%

☒ 66.67%

Previous Question

Next Question

ASUS VivoBook

Service providers	Jan'2012	Feb'2012	Mar'2012
SuperCab	16	15	16
TravelHome	19	18	20
One Call	15	18	18
Drive Home	14	15	12
King Cab	18	16	17
Others	18	18	17
Total	100	100	100

Question:

How much revenue is generated by the 'King Cab' in the month of January 2012, if the total revenue of the market in month of January is Rs. 27.5 million?

☐ Rs. 4.25 million

☐ Rs. 5.25 million

☐ Rs. 4.5 million

☒ Rs. 4.65 million

Previous Question

Next Question

ASUS VivoBook

5

6

7

8

9

10 ☆

11

12

13

14

15

QUESTION: 10 GROUP: Aptitude SECTION: Puzzles

Marks: 1

How many such pairs of letters are there in the word "PREHENSION" which has as many letters between them (from both the sides) as in the alphabet from A to Z?

2

4

5

3

forward-(H,N)
backward-(n,o),(n,r),(i,p)

Previous Question

Next Question

ASUS VivoBook

1

2 ☆

3

4

5

6

7

8

9

10

11

12

- (I) Ajit's last name is not Pandey but he is a Network engineer and he does not play either Violin or Piano.
- (II) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (III) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (IV) Java developer is working in Chennai and his name is not Pankaj.
- (V) Singh does not play Flute.
- (VI) The person who is working in Chennai plays Piano.

Question:

If Pankaj and Ajit interchange last name then what is the last name of Pankaj?

☐ Singh

☒ Sha

☐ Naik

☐ Pandey

Previous Question

Next Question

ASUS VivoBook

- (I) Ajit's last name is not Pandey but he is a Network engineer and he lives in Bangalore.
- (II) Net developer's last name is Naik and he is not working in Bangalore but he plays Violin.
- (III) Sunil is a Test engineer and he is not working in either Bangalore or Hyderabad and his last name is not Sha or Singh.
- (IV) Java developer is working in Chennai and his name is not Pankaj.
- (V) Singh does not play Flute.
- (VI) The person who is working in Chennai plays Piano.

Question:

Which of the following is true?

- ☐ Ajit - Bangalore - Violin
- ☐ Pankaj - Jaipur - Violin
- ☐ Sunil - Jaipur - Flute
- ☒ Amit - Chennai - Piano

Previous Question

Next Question

ASUS VivoBook

QUESTION: 7 GROUP: Aptitude SECTION: Data Analysis
Mark(s): 1

Direction: Answer the question based on the information given below.

XYZ is one of the most visited city of the world attracts big crowd of tourist. There are five major competitors in the city who provides cab service to the tourists.

The following table gives detail about the percentage share of the service providers for the three months in the total market.

Service providers	Jan'2012	Feb'2012	Mar'2012
Super Cab	16	15	16
Travel Home	19	18	20
One Call	15	18	18
Drive Home	14	15	12
King Cab	18	16	17
Others	18	18	17
Total	100	100	100

Question:

How much revenue is generated by the 'King Cab' in the month of January 2012, if the total revenue of the market in month of January is Rs. 27.5 million?

Previous Question

Next Question

ASUS VivoBook

33

34

35

36

37

38 ☆

39

40

41

42

43

Previous Question

Next Question

ASUS VivoBook

29

QUESTION 34 GROUP: Hardware SECTION: RTL

Mark(s): 1

30

Operation diagram of a RTL is shown in figure.

31

32

33

34 ☆

35


36

37

38

39

40

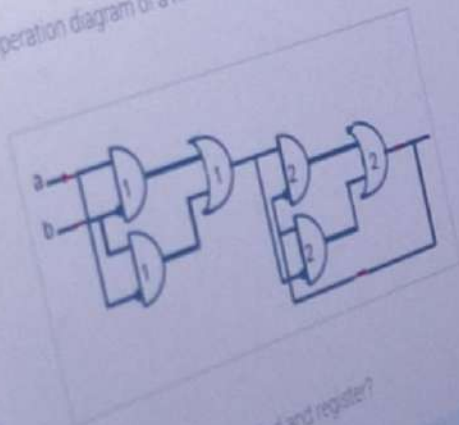

Calculate the clock period and register?

Clock period = 4
And register = 4

Clock period = 8
And register = 3

Previous Question

Next Question

ASUS VivoBook

29

30

31

32

33

34 ☆

35

36

37

38

39

Calculate the clock period and register?

☒ Clock period = 4
And registers = 3

☐ Clock period = 8
And registers = 3

☐ Clock period = 6
And registers = 4

☐ Clock period = 7
And registers = 3

Previous Question

Next Question

ASUS VivoBook

30

31

32

33

34

35 ☆

36

37

38

39

40

QUESTION: 35 GROUP: Hardware SECTION: VLSI

Mark(s): 1

Which of the following is the simplified form of the expression $((c \rightarrow b) \rightarrow ((a \vee c) \rightarrow b))$?

☐ $b \rightarrow a$

☒ $a \rightarrow b$

☐ $c \rightarrow a$

☐ $a \rightarrow c$

Previous Question

Next Question

ASUS VivoBook

28

29

30

31

32

33 ☆

34

35

36

37

38

QUESTION: 33 GROUP: Hardware SECTION: VLSI

Mark(s): 1

Which of the following process technology is not used in FPGA?

☐ EPROM

☐ Anti Fuse

☐ EEPROM

☐ SRAM

Previous Question

Next Question

ASUS VivoBook

27

28

29

30

31

32 ☆

33

34

35

36

37

QUESTION: 32 GROUP: Hardware SECTION: Semiconductor Physics

Mark(s): 1

For a silicon semiconductor the Temperature was increased to 64 times the room temperature. If the intrinsic concentration n_i at room temperature is $1.5 \times 10^{10} \text{ cm}^{-3}$, what is the value of n_i at the increased temperature?

☐ $96 \times 10^{10} \text{ cm}^{-3}$

☒ $3 \times 10^{10} \text{ cm}^{-3}$

☐ $12 \times 10^{10} \text{ cm}^{-3}$

☐ $6 \times 10^{10} \text{ cm}^{-3}$

Previous Question

Next Question

ASUS VivoBook

QUESTION: 31 GROUP: Hardware SECTION: Microprocessors and Microcontrollers

Mark(s): 1

What is the value of single phase clock frequency of an 8085 microprocessor?

☒ 3.2 MHz

☐ 3 MHz

☐ 3.5 MHz

☐ 2.5 MHz

Previous Question

Next Question

ASUS VivoBook

25

26

27

28

29

30 ☆

31

32

33

34

35

QUESTION: 30 GROUP: Hardware SECTION: VLSI

Mark(s): 1

Which technology is generally not available for use in FPGA?

☐ SRAM

☐ Anti-fuse

☐ EPROM

☒ DRAM

Previous Question


Next Question

ASUS VivoBook

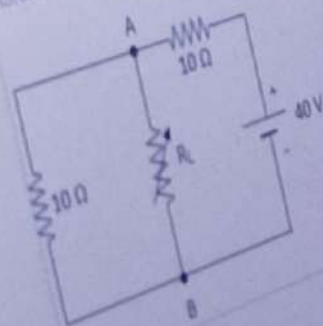QUESTION 27 GROUP Hardware SECTION: Basic Electronics

Mark(s): 1

In the following circuit, if the value of Thevenin's resistance R_{Th} between open-circuited terminals A-B is 5 Ω , the maximum power transferred to the load R_L will be:



30 W

20 W

15 W

10 W

Previous Question

New Question

ASUS VivoBook

24

QUESTION: 29 GROUP: Hardware SECTION: RTL

Mark(s): 1

25

26

27

28

29 ☆

30

31

32

33

34

If the propagation delay of RTL-NOR gate is 500ns, then is the RTL-NOR gate can work at the speed of 4MHz?


☐ It can work because its Fan in is 7☐ It cannot work because its propagation delay is very low (in ns)☒ It cannot work because its propagation delay is very High (in ns)☐ It can work because its Fan out is 7[Previous Question](#)[Next Question](#)

ASUS VivoBook

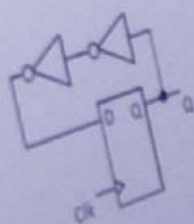QUESTION 26 GROUP: Hardware SECTION: RTL

Mark(s): 1

Below is the circuit consisting of one D flip-flop and two inverters in cascade. If t_{setup} is the inverter delay and t_{prop} is propagation delay, set-up time and hold time of flip-flop respectively then what should be the minimum clock period?



☐ $T \leq t_{\text{setup}} + 2t_{\text{prop}}$

☐ $T \leq t_{\text{setup}} + 2t_{\text{prop}} + t_{\text{hold}}$

☐ $T \geq t_{\text{setup}} + 2t_{\text{prop}}$

☐ $T \geq t_{\text{setup}} + 2t_{\text{prop}} + t_{\text{hold}}$

Previous Question

Next Question

ASUS VivoBook

24

QUESTION: 29 GROUP: Hardware SECTION: RTL

Mark(s): 1

25

26

27

28

29 ☆

30

31

32

33

34

If the propagation delay of RTL-NOR gate is 500ns, then is the RTL-NOR gate can work at the speed of 4MHz?

- ☐ It can work because its Fan in is 7
- ☐ It cannot work because its propagation delay is very low (in ns)
- ☐ It cannot work because its propagation delay is very High (in ns)
- ☐ It can work because its Fan out is 7


[Previous Question](#)[Next Question](#)

ASUS VivoBook

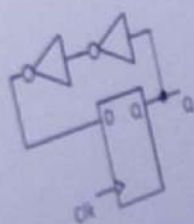QUESTION 26 GROUP: Hardware SECTION: RTL

Mark(s): 1

Below is the circuit consisting of one D flip-flop and two inverters in cascade. If t_{setup} is the inverter delay and t_{prop} is propagation delay, set-up time and hold time of flip-flop respectively then what should be the minimum clock period?



☐ $T \leq t_{\text{setup}} + 2t_{\text{prop}}$

☐ $T \leq t_{\text{setup}} + 2t_{\text{prop}} + t_{\text{hold}}$

☐ $T \geq t_{\text{setup}} + 2t_{\text{prop}}$

☐ $T \geq t_{\text{setup}} + 2t_{\text{prop}} + t_{\text{hold}}$

Previous Question

Next Question

ASUS VivoBook

21

QUESTION: 25 GROUP: Hardware SECTION: Microprocessors and Microcontrollers
Mark(s): 1

22

For 8051 microcontroller what will happen when the accumulator is assigned the value as MOV A, 3FEH?

23

☐ Will result in an error as the value is greater than FF H.

24

☐ The value 3FE H will be moved to Accumulator.

25 ☆

☐ The value FE H will be moved to accumulator.

26

☐ The value at address 3FE H will be moved to accumulator.

27

28

29

30


[Previous Question](#)[Next Question](#)

ASUS VivoBook

QUESTION 28 GROUP: Hardware SECTION: Digital Electronics

Marks: 1

The following circuit represent a-

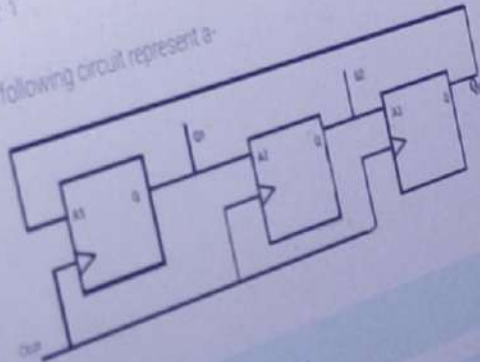

Asynchronous decade Counter

Synchronous Ring Counter

Asynchronous Johnson Counter

Asynchronous binary Counter

Previous Question

Next Question

ASUS VivoBook

21 ☆

QUESTION: 21 GROUP: Hardware SECTION: Digital Electronics
Mark(s): 1

22

Simplify the Boolean algebra:
 $XY + X(Y+Z) + Y(Y+Z)$

23

24

☒ $Y+XZ$

25

☐ $YY+XZ$

26

☐ $ZY+XZ$

27

☐ $ZX+ZY$

28

29

30

Previous Question

Next Question

ASUS VivoBook

QUESTION 22 GROUP: Hardware SECTION: Analog Circuits

Mark(s) 1

For N-channel enhancement mode MOSFET conduction, which of the relation holds true for the gate-to-source voltage (V_{GS})?

☐ $V_{GS} < 0$

☐ $V_{GS} = 0$


☐ V_{GS} less than V_{th}

☒ V_{GS} equal to or greater than V_{th}

Previous Question

Next Question

ASUS VivoBook

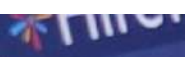

QUESTION: 23 GROUP: Hardware SECTION: Verilog

Marks: 1

In a Verilog Module, input, output, inout wires of the ports are defined as

input[7:0] data;
output[3:0] out;
inout cont;

What does it mean?

☐ 8 bit input "data" port, 4 bit output "out" port and uni-directional "cont" wire

☐ 4 bit input "data" port, 8 bit output "out" port and uni-directional "cont" wire

☒ 8 bit input "data" port, 4 bit output "out" port and bi-directional "cont" wire

☐ 4 bit input "data" port, 8 bit output "out" port and bi-directional "cont" wire

Previous Question


Next Question

ASUS VivoBook

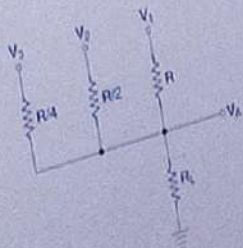QUESTION: 49 GROUP: Hardware SECTION: Digital Electronics

Mark(s): 1

A resistive divider type DAC has resistors $R, R/2, R/4$ and so on. If the resistors of a 3-bit resistive divider are fed with voltages V_1, V_2 and V_3 and the analog output voltage is 12V find the value of voltage fed to $R/4$ resistor.



14 V

21 V

28 V

7 V

Previous Question


Next Question

ASUS VivoBook

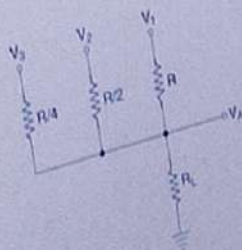QUESTION: 49 GROUP: Hardware SECTION: Digital Electronics

Mark(s): 1

A resistive divider type DAC has resistors R , $R/2$, $R/4$ and so on. If the resistors of a 3-bit resistive divider are fed with voltages V_1 , V_2 and V_3 and the analog output voltage is 12V find the value of voltage fed to $R/4$ resistor.



14 V

21 V

28 V

7 V

Previous Question

Next Question

ASUS VivoBook